

B. E. First Semester (ALL) / SOE – 18-19 – Rev – FY-201 Examination

Course Code : EL 2101

Course Name : Electrical Engineering

Time : 2 Hours]

[Max. Marks : 40

Instructions to Candidates :—

- (1) Attempt any **Four** questions out of **Six**.
- (2) All questions carry **Ten** marks.
- (3) Assume suitable data wherever necessary.
- (4) Diagrams should be given wherever necessary.
- (5) Illustrate your answers wherever necessary with the help of neat sketches.
- (6) Use of non programmable calculator is permitted.

1. Solve **Q. 1 (A)** or **Q. 1 (B)** :—

- (A) (A1) Determine the current through 1Ω resistor in the network shown in Fig. 1, use mesh analysis.

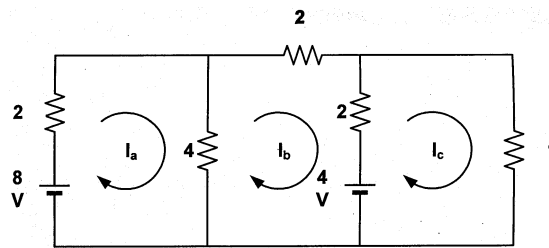


Fig. 1

6(CO2)

- (A2) Calculate R_{ab} for the circuit shown in Fig. 2.

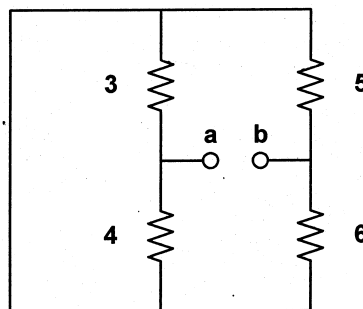


Fig. 2

4(CO2)

- (B) (B1) For the circuit of Fig. 3, compute the voltage across each current source.

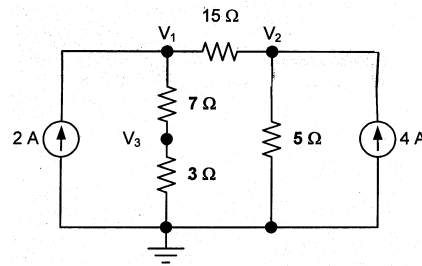


Fig. 3

6(CO2)

- (B2) Find V_{AB} in Fig. 4 by using superposition theorem.

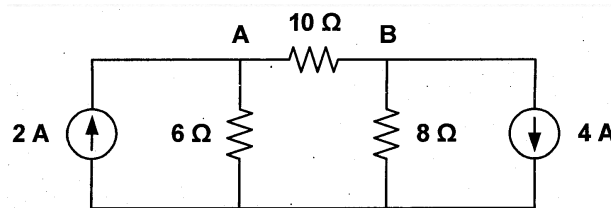


Fig. 4

4(CO2)

2. Solve Q. 2 (A) or Q. 2 (B) :—

- (A) (A1) A series R–L circuit, having $R=4\Omega$ and $L=0.2\text{ H}$ is connected across $230 \angle 30^\circ \text{ V}$, 50 Hz supply. Calculate :

- The current drawn by the circuit, and
- The power factor of the circuit.

4(CO2)

- (A2) Calculate the average and r.m.s. value of the voltage waveform shown in Fig.5. Also show that form factor and peak factor are equal to one.

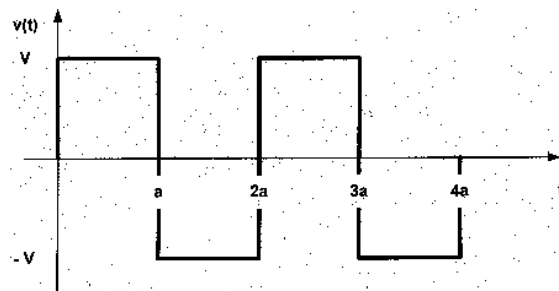


Fig. 5

6(CO2)

- (B) (B1) A coil has an inductance of 0.05 H and a resistance of 10Ω . It is connected to a sinusoidal 200 V, 50 Hz supply. Calculate the impedance, current, power consumed and power factor. 4(CO2)

- (B2) The instantaneous voltages across each of the three coils connected in series is given by

$$v_1(t) = 200 \sin(\omega t)$$

$$v_2(t) = 200 \sin(\omega t - 120^\circ)$$

$$v_3(t) = 200 \sin(\omega t + 120^\circ)$$

Determine an expression for the resultant voltage $v(t)$. 6(CO2)

3. Solve **Q. 3 (A)** or **Q. 3 (B)** :

- (A) (A1) A 60Ω resistor is connected in parallel with an inductive reactance of 80Ω to a 240 V, 50 Hz supply. Calculate :

- (i) The current through the resistor and inductive reactance ;
- (ii) The supply current ;
- (iii) The circuit phase angle ;
- (iv) Power factor ;
- (v) P, Q, and S. 6(CO2)

- (A2) Three impedances $(6 + j5)\Omega$, $(8 - j6)\Omega$ and $(8 - j10)\Omega$ are connected in parallel. Calculate the current in each branch when the total current is 20 A. 4(CO2)

- (B) (B1) The following single-phase loads are connected to a 230 V supply :

160 kVA at 0.7 power factor lagging

50 kVA at 0.65 power factor leading

50 kW at unity power factor

Calculate :

- (i) The total load in kVA ;
- (ii) The line current ;
- (iii) The combined power factor. 6(CO2)

- (B2) A 10Ω resistor, a 15.9 mH inductor and a $159\mu\text{F}$ capacitor are connected in parallel to a 200 V, 50 Hz supply. Calculate the supply current and power factor. 4(CO2)

4. Solve **Q. 4 (A)** or **Q. 4 (B)** :

- (A) (A1) A balanced star-connected load of $(4 + j3) \Omega$ per phase is connected to a 3-phase, 415-V, 50-Hz supply.

Find :

- (i) The line current,
- (ii) The power factor,
- (iii) The power,
- (iv) The reactive volt-ampere, and
- (v) The total volt-ampere.

6(CO2)

- (A2) Three identical resistors each of value 40Ω are connected first in star and then in delta across a 200 V, three-phase, 50 Hz supply. Calculate the power taken from the supply in each case. 4(CO2)

- (B) (B1) Each phase of a delta connected load has a resistance of 25Ω , an inductance of 0.15 H , and a capacitance of $120 \mu\text{F}$. The load is connected across a 400 V, 50 Hz three-phase supply. Determine the line current, volt-ampere, active power and reactive volt-ampere. 6(CO2)

- (B2) Three identical resistors of 20Ω are connected in star to a 415 V, three phase, 50 Hz supply.

- (i) Calculate the total power taken by the load.
- (ii) Also calculate the power consumed in the resistors if they are connected in delta to the same supply. 4(CO2)

5. Solve **Q. 5 (A)** or **Q. 5 (B)** :

- (A) (A1) A 200 kVA, single phase transformer with a voltage ratio 6350/660 V has the following winding resistances and reactances :

$$R_1 = 1.56 \Omega \quad R_2 = 0.016 \Omega$$

$$X_1 = 4.67 \Omega \quad X_2 = 0.048 \Omega$$

Calculate the resistance and reactance of the transformer referred to the high-voltage and low-voltage winding. 5(CO4)

(A2) A 2 kVA, 400/200 V, 50 Hz, single phase transformer has the following parameters as referred to primary side :

$$R_{e1} = 3 \, \Omega ; X_{e1} = 4 \, \Omega$$

Determine the regulation of transformer, when operating at :

- (i) Full load with 0.8 p.f. lagging ;
- (ii) Full load with 0.8 p.f. leading ;
- (iii) Half load at 0.8 p.f. lagging. 5(CO4)

(B) (B1) In a transformer, the core loss is found to be 52 W at 40 Hz ; and 90 W at 60 Hz : measured at same peak flux density. Compute the hysteresis and eddy current losses at 50 Hz. 5(CO4)

(B2) A 20 kVA, 1100/110-V transformer has primary and secondary winding resistances of $4.0 \, \Omega$ and $0.04 \, \Omega$, respectively. If the core loss is 2.5 kW, determine the efficiency of the transformer when it is delivering :

- (i) Full load and
- (ii) Half load at 0.8 power factor. Calculate the load at which the transformer has maximum efficiency. What is the maximum efficiency of the transformer ? 5(CO4)

6. Solve **Q. 6 (A)** or **Q. 6 (B)** :

(A) (A1) Derive torque equation of a three phase induction motor. 5(CO3)

(A2) A 4 pole induction motor is fed from 50 Hz supply, and has a rotor speed of 1425 r.p.m. Find :

- (i) Slip speed ;
- (ii) Per unit slip ;
- (iii) Percent slip. 5(CO4)

(B) (B1) Give comparison between squirrel cage induction motor and slip ring induction motor. (write any three points of comparison). 5(CO3)

(B2) A 4 pole, 3 phase induction motor operates from a supply whose frequency is 50 Hz. Calculate :

- (i) The speed at which the magnetic field of the stator is rotating ;
 - (ii) The speed of the rotor when the slip is 0.04 ;
 - (iii) The frequency of the rotor current when the slip is 0.03.
- 5(CO4)

