

**B. E. First Semester (All) / SoE–2018-19 Examination**

**Course Code : EE 2101**

**Course Name : Basic Electronics**

Time : 3 Hours ]

[ Max. Marks : 60

**Instructions to Candidates :—**

- (1) All questions are compulsory.
- (2) All questions carry marks as indicated.
- (3) Due credit will be given to neatness and adequate dimensions.
- (4) Assume suitable data wherever necessary.
- (5) Diagrams and chemical equations should be given wherever necessary.
- (6) Illustrate your answers wherever necessary with the help of neat sketches.

1. (A1) Perform the BCD Arithmetic :

$$(679.6)_{10} + (536.8)_{10}$$

$$(123.4)_{10} + (567.8)_{10} \quad 4 \text{ (CO 1)}$$

(A2) Convert :

$$(i) (101111011.110)_2 = (?)_{10}$$

$$(ii) (134.443)_5 = (?)_9 \quad 3 \text{ (CO 1)}$$

(A3) Perform using 1's complement method :

$$(i) \text{ Subtract } (11)_2 \text{ from } (110010)_2$$

$$(ii) \text{ Subtract } (1100010)_2 \text{ from } (101)_2 \quad 3 \text{ (CO 1)}$$

**OR**

(B1) A and B are two successive digits in a certain number system. When written as AB it becomes  $[41]_{10}$  and when written as BA it becomes  $[49]_{10}$ . Find the base of the system and values of A and B. 4 (CO 1)

(B2) Perform signed number Arithmetic using 2's complement :

$$(i) (-85)_{10} + (-39)_{10}$$

$$(ii) (-97)_{10} - (-104)_{10} \quad 3 \text{ (CO 1)}$$

(B3) Convert octal number into its equivalent gray code :

$$(1001111010)_8 \quad 3 \text{ (CO 1)}$$

2. (A1) Design X–OR Gate using NAND and NOR gates only. 3 (CO 1)

(A2) Simplify the following expression using Boolean Algebra :

$$A = XY + (XZ)' + XY'Z'(XY + Z) \quad 3 \text{ (CO 1)}$$

(A3) Design Half Subtractor Circuit implement using NAND Gate Only.

4 (CO 1)

**OR**

(B1) Design S–R Flip Flop and Explain with Truth Table. 5 (CO 1)

(B2) Design full adder circuit with gate level implementation. 3 (CO 1)

(B3) Reduce the expression using Boolean Algebra :

$$F = (B + BC) (B + B'C) (B + D) \quad 2 \text{ (CO 1)}$$

3. (A1) Explain Intrinsic and Extrinsic Semiconductor with crystal structure.

3 (CO 2)

(A2) Explain Unbiased P–N junction in detail.

4 (CO 2)

(A3) For what values of reverse voltage will the reverse current reach 90% of its saturation value at room temperature ? Assume Si p–n junction diode.

3 (CO 2)

**OR**

(B1) What is Rectifier ? Explain center tapped Full wave Rectifier with Input Output Waveform and derive the equation for  $I_{dc}$ ,  $V_{dc}$  and Efficiency.

4 (CO 2)

(B2) Explain working of Common emitter configuration with its input and output characteristics.

4 (CO 2)

(B3) What is MOSFET ? Write its type.

2 (CO 2)

4. (A1) Draw and Explain Adder and Subtractor circuit using OPAMP. 5 (CO 3)

(A2) Draw and explain the Non-Inverting amplifier using OP-Amp. 3 (CO 3)

(A3) What do you mean by Slew Rate of OP-AMP ? 2 (CO 3)

**OR**

(B1) Explain the concept of virtual ground. 3 (CO 3)

(B2) Draw and explain differentiator using Op-amp. Also derive the expression for output voltage. 3 (CO 3)

(B3) Draw the circuit diagram using OP-AMP for given expression.  
 $V_0 = -R_f/R_1(V_1 + V_2 + V_3)$  and derive  $V_0 = (1 + R_f/R_1)(V_1 + V_2 + V_3)$   
4 (CO 3)

5. (A1) A circuit of tuned for resonance by eight different students and the value of resonant frequency in kHz were recorded as : 552, 548, 543, 535, 546, 531, 543, 536.

Calculate :

(i) Arithmetic mean.

(ii) Deviation from mean.

(iii) The average deviation.

(iv) Standard deviation. 5 (CO 4)

(A2) Describe the balance condition equation for Maxwell's bridge. 3 (CO 4)

(A3) What are different standards of measurement ? Give their classification in brief. 2 (CO 4)

**OR**

(B1) Define Accuracy, Reproducibility, Precision and Sensitivity with respect to measurement. 4 (CO 4)

(B2) Describe the balance condition equation for Schering's bridge. 3 (CO 4)

(B3) What are three general classes of error ? With examples discuss the means adopted to minimize error. 3 (CO 4)

6. (A1) Explain Thermocouple in detail. 4 (CO 4)  
(A2) Explain the Proximity Sensors with neat diagram. 3 (CO 4)  
(A3) Derive the expression for gauge factor of a strain gauge. 3 (CO 4)

**OR**

- (B1) Explain the working of LVDT in detail. 4 (CO 4)  
(B2) Define load cell and explain its types. 3 (CO 4)  
(B3) Explain the bonded type strain gauges. 3 (CO 4)