

**B. E. First Semester (All)/SoE–2018-19 Examination****Course Code : EL 2101****Course Name : Electrical Engineering**

Time : 3 Hours]

[Max. Marks : 60

**Instructions to Candidates :—**

- (1) All questions are compulsory.
- (2) All questions carry marks as indicated.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.
- (5) Use of non – programmable calculator, Drawing instruments is permitted.

1. Solve any **Two** of the following :

- (a) Find the equivalent resistance of the circuit shown in Fig. 1 between the points A and B. Each resistor has a resistance 'r'.

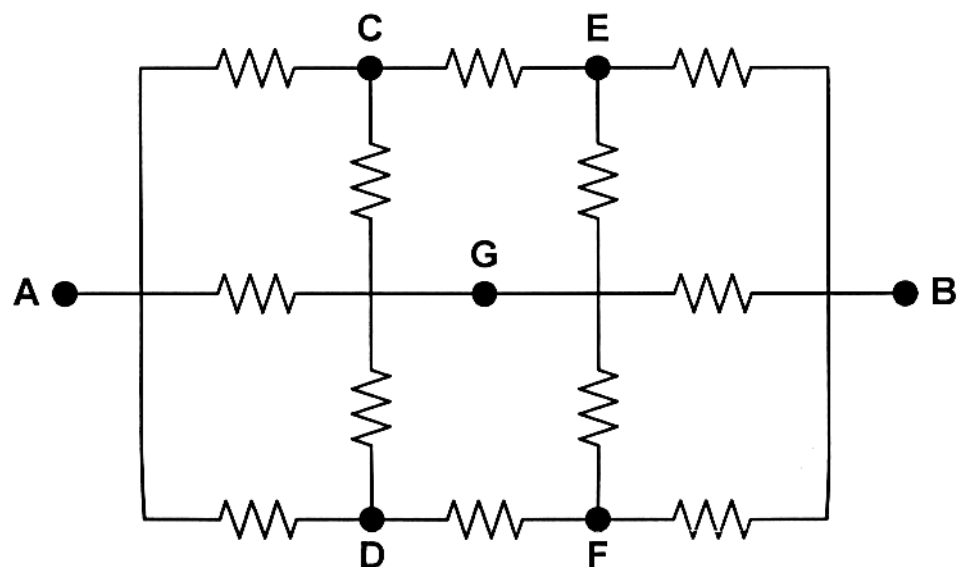


Fig. 1

5CO2)

(b) In the network shown in Fig. 2, determine :

- (i) The current  $I$ ;
- (ii) Voltage across  $5\ \Omega$  resistor;
- (iii) Power loss in  $18\ \Omega$  resistor.

Use Ohm's law and current division rule.

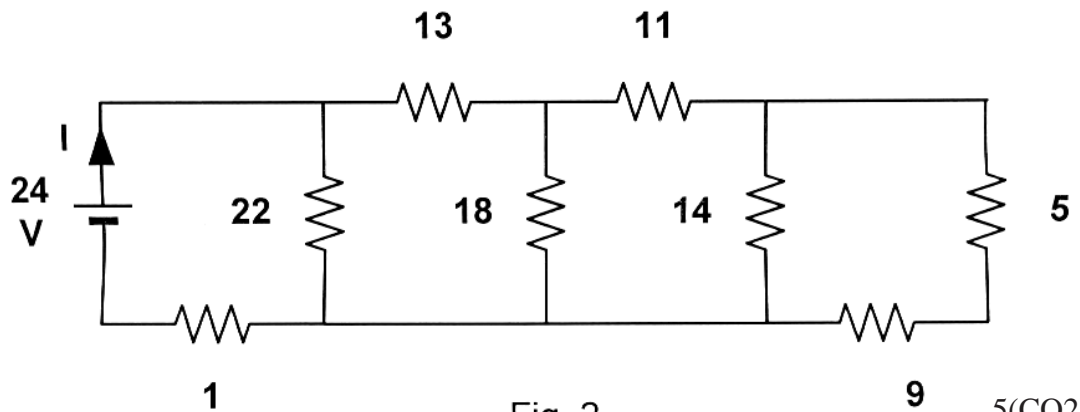


Fig. 2

5(CO2)

(c) Find the current through  $20\ \Omega$  resistor in the network shown in Fig. 3. Use mesh analysis.

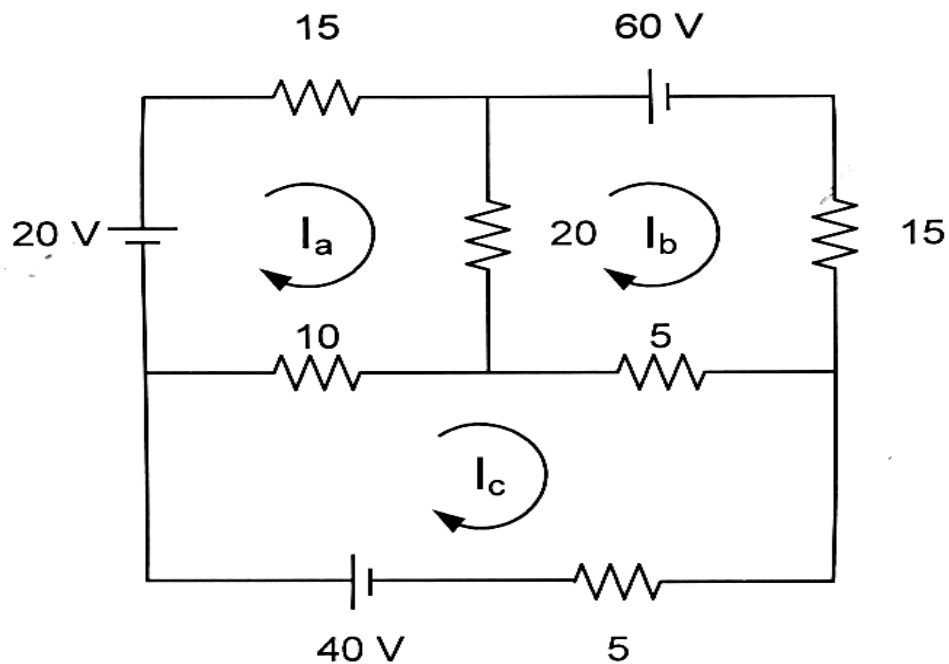


Fig. 3

5(CO2)

2. Solve any **Two** of the following :

- (a) Calculate the average value and r.m.s. value of the function shown in Fig.4.

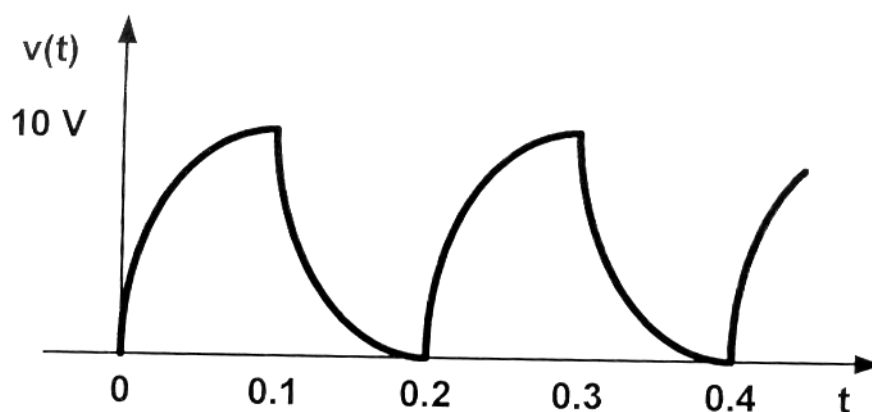


Fig. 4

It is given that

$$y(t) = \begin{cases} 10(1 - e^{-100t}) & 0 < t < 0.1 \\ 10e^{-50(t-0.1)} & 0.1 < t < 0.2 \end{cases} \quad 5(\text{CO2})$$

- (b) In the circuit of Fig 5,  $v_s(t) = 120\cos(377t+90^\circ)$ ,  $v_1(t) = 40\sqrt{2} \cos(377t+45^\circ)$ , and  $v_3(t)=60\cos (377t-53.13^\circ)$ . Find an expression for the voltage  $v_2(t)$ .

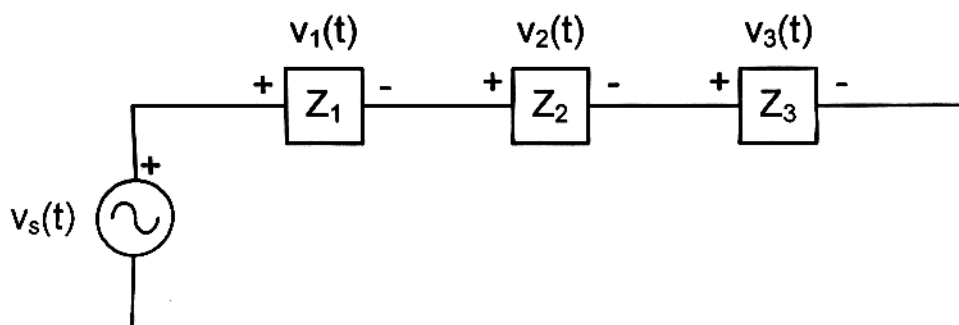


Fig.5

5(CO2)

- (c) A series R–C circuit, having  $R = 4\ \Omega$  and  $C = 120\ \mu\text{F}$ , is connected across 230 V, 50 Hz supply.  
Calculate :
- (i) The reactance,
  - (ii) The impedance,
  - (iii) The current drawn by the circuit, and,
  - (iv) The power factor of the circuit. 5(CO2)

3. Solve any **Two** of the following :

- (a) Two circuits, the impedances of which are given by  $\bar{Z}_1 = 10 + j15\ \Omega$  and  $\bar{Z}_2 = 6 - j8\ \Omega$  are connected in parallel. If the total current supplied is 15 A, what is the power taken by each branch ? 5(CO2)
- (b) Four loads are connected across a 230 V, 50 Hz line :
- Lights 10 kVA at unity power factor.  
A motor 4 kW at power factor 0.8 lagging.  
A rectifier 3.6 kW at power factor 0.6 leading.  
A capacitor of 8 kVA.  
Determine :
- (i) The total kW;
  - (ii) The total kVAr;
  - (iii) The total kVA;
  - (iv) The overall power factor;
  - (v) The total line current. 5(CO2)
- (c) Two inductive coils A and B are in parallel across a 100 V, 50 Hz supply. Coil A takes 12 A at 0.9 power factor and the total current for both the coils is 20 A at 0.8 power factor.  
Determine :
- (i) The equivalent resistance and equivalent reactance;
  - (ii) The individual resistance and reactance of both coils;
  - (iii) The power factor of coil B. 5(CO2)

4. Solve any **Two** of the following :

- (a) A balanced star-connected load of  $(4 + j3)\Omega$  per phase is connected to a 3-phase, 415 – V, 50 – Hz supply.

Find :

- (i) The line current,
- (ii) The power factor,
- (iii) The power,
- (iv) The reactive volt-amperes, and
- (v) The total volt amperes.

5(CO2)

- (b) A delta connected load draws a current of 15 A at a lagging power factor of 0.85 from a 400 V, 3-phase, 50 Hz supply. Find the resistance and inductance of each phase.

5(CO2)

- (c) A three-phase delta-connected load, each phase of which has an inductive reactance of  $40\Omega$  and a resistance of  $25\Omega$ , is fed from the secondary of a three-phase star-connected transformer, which has a phase voltage of 240 V. Draw the circuit diagram of the system and calculate :

- (i) The current in each phase of the load;
- (ii) The p.d. across each phase of the load;
- (iii) The current in the transformer secondary windings;
- (iv) The total power taken from the supply and its power factor.

5(CO2)

5. Solve any **Two** of the following :

- (a) The following results were obtained on a 50 kVA, 2400/120 V transformer:

Open circuit test, instruments on L. V. side : 396 W, 9.65 A, 120 V

Short circuit test, instruments on H. V. side : 810 W, 20.8 A, 92 V

Determine :

- (i) The circuit constants :
- (ii) The efficiency at full load, 0.8 power factor lagging;

(iii) The approximate voltage regulation. 5(CO3)

- (b) A 20 kVA, 1100/110 V transformer has primary and secondary winding resistances of  $4.0\ \Omega$  and  $0.04\ \Omega$ , respectively. If the core loss is 2.5 kW, determine the efficiency of the transformer when it is delivering :

(i) Full load and, (ii) Half load at 0.8 power factor.  
Calculate the load at which the transformer has maximum efficiency.  
What is the maximum efficiency of the transformer ? 5(CO3)

- (c) A 2 kVA, 400/200 V, 50 Hz, single phase transformer has the following parameters as referred to primary side :

$$R_{e1} = 3\ \Omega; X_{e1} = 4\ \Omega$$

Determine the regulation of transformer, when operating at :

- (i) Full load with 0.8 p.f. lagging;  
(ii) Full load with 0.8 p.f. leading;  
(iii) Half load at 0.8 p.f. lagging. 5(CO3)

6. Solve any **Two** of the following :

- (a) Write advantages, disadvantages and application of three phase induction motor. 5(CO3)

- (b) Give comparison between squirrel cage induction motor and slip ring induction motor. 5(CO3)

- (c) A three phase, 400 V, 50 Hz induction motor has a speed of 950 r.p.m. on full load. The motor has 6 poles.  
Calculate :

- (i) How many complete alternations will the rotor voltage make per second ?  
(ii) Speed of rotor field with respect to rotor core. 5(CO3)