

B. E. First Semester (All)/ SoE–2018-19 Examination

Course Code : EE 2101

Course Name : Basic Electronics

Time : 3 Hours]

[Max. Marks : 60

Instructions to Candidates :—

- (1) All questions are compulsory.
- (2) All questions carry marks as indicated.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.

1. (A) Solve any **One** :

(A1) The equation $5x^2 - 14x - 226 = 0$ has the root 9, -6. Find the base of the system. 4(CO1)

(A2) Perform using BCD Arithmetic :

(i) $(457.56)_{10} + (984.56)_{10}$

(ii) $(800.01)_{10} - (199.8)_{10}$ 4(CO1)

(B) Solve any **One** :

(B1) Convert Gray code into its equivalent octal and decimal numbers $(1011010101101011)_{\text{gray}}$. 3(CO1)

(B2) Convert octal number into its equivalent gray code $(2514)_8$. 3(CO1)

(C) Solve any **One** :

(C1) Perform signed number Arithmetic using 2's complement.

(i) $(-121)_{10} + (+98)_{10}$

(ii) $(-89)_{10} - (-78)_{10}$ 3(CO1)

(C2) Perform using 1's complement method.

(i) Subtract $(11)_2$ from $(110010)_2$

(ii) Subtract $(1100010)_2$ from $(101)_2$ 3(CO1)

2. (A) Solve any **One** :
- (A1) Design half adder circuit with gate implementation. 3(CO1)
- (A2) Design Half Subtractor Circuit implement using logic Gates. 3(CO1)
- (B) Solve any **One** :
- (B1) Draw AND–OR logic circuit for the expression $Y = AB + AC$ and replace the AND–OR circuit by NAND circuit. 4(CO1)
- (B2) State DeMorgan's Theorem and use it to simplify the following expression.
- $$\overline{\overline{(A+B)} + \overline{(C+D)}}$$
- 4(CO1)
- (C) Solve any **One** :
- (C1) What is D Flip Flop ? Explain with Truth Table. 3(CO1)
- (C2) Explain T Flip Flop with truth table. Draw Gate level Diagram. 3(CO1)
3. (A) Solve any **One** :
- (A1) Explain PN junction diode with its characteristics. 4(CO2)
- (A2) What is Rectifier ? Explain center tapped Full wave Rectifier with Input Output Waveform and derive the equation for I_{dc} , V_{dc} and Efficiency. 4(CO2)
- (B) Solve any **One** :
- (B1) A Ge diode has a reverse saturation current of $3\mu A$. Calculate the voltage at which 1% of the rated current will flow through the diode, at room temperature if diode is rated for 1A. 3(CO2)
- (B2) If the reverse saturation current in a PN junction diode is 5 nA, find the applied voltage for a forward current of $0.68\mu A$. Assume silicon diode. 3(CO2)

(C) Solve any **One** :

(C1) Explain the working of NPN transistor. 3(CO2)

(C2) Explain working of Common emitter configuration with its input and output characteristics. 3(CO2)

4. (A) Solve any **One** :


(A1) Draw and explain Block diagram of OP-AMP. 4(CO3)

(A2) List ideal characteristics of OP-AMP (any 8) 4(CO3)

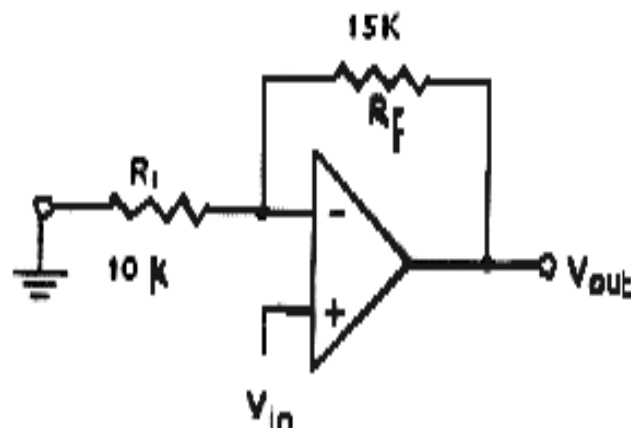(B) Solve any **One** :

(B1) Draw and explain summing Amplifier using OP-AMP and also derive its output equation. 3(CO3)

(B2) What is the range of the output voltage in the circuit of fig. if the input varies from 0.1 to 0.5 V ?




3(CO3)

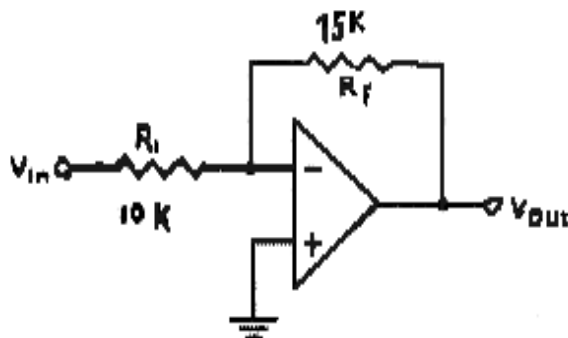(C) Solve any **One** :

(C1) Draw and explain the Non-Inverting amplifier using OP-Amp and also derive its output equation. 3(CO3)

- (C2) What is the range of the output voltage in the circuit of fig. if the input resistance is a potentiometer that varies from 10k to 20K and V_{in} is 1V ?



3(CO3)

5. (A) Solve any **One** :

(A1) The following 8 observations were recorded when measuring a voltage :

41.7, 42.0, 41.8, 42.0, 42.1, 41.9, 42.5 and 41.8 Volts.

Find

- (i) The mean.
- (ii) The standard deviation.
- (iii) Average deviation.
- (iv) Variance.

4(CO4)

(A2) A circuit has turned for resonance by eight different students and the value of resonant frequency in kHz were recorded as 552, 548, 543, 535, 546, 531, 543 and 536.

Calculate :

- (i) Arithmetic mean.
- (ii) The average deviation.
- (iii) Standard deviation.
- (iv) Variance.

4(CO4)

- (B) Solve any **One** :
- (B1) What are different standards of measurement ? Give their classification in brief. 3(CO4)
- (B2) Explain various types of errors in detail. 3(CO4)
- (C) Solve any **One** :
- (C1) Derive the balance condition equation for Maxwell's inductance. 3(CO4)
- (C2) Describe the balance condition equation for Schering's bridge. 3(CO4)
6. (A) Solve any **One** :
- (A1) How are transducers classified ? Give examples. 4(CO4)
- (A2) Define load cell and explain its types. 4(CO4)
- (B) Solve any **One** :
- (B1) Explain the working of LVDT in detail. 4(CO4)
- (B2) Explain the Proximity Sensors with neat diagram. 3(CO4)
- (C) Solve any **One** :
- (C1) Explain Thermocouple in detail. 3(CO4)
- (C2) Explain Thermistor in detail. 3(CO4)